



Physics: Required Practical 2




- 🍏 What is this required practical about?
-

- 🍏 Draw a circuit diagram to show how this piece of equipment (above) is put into a circuit.
Also include: one battery, one voltmeter, one ammeter, one bulb

- 🍏 Think about how you carried out this practical.

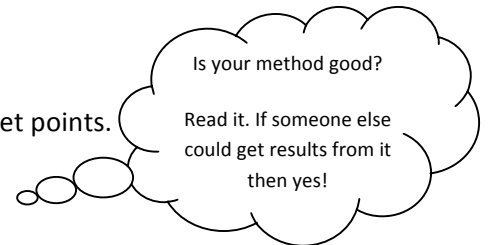Write a logical and comprehensive method, using numbered bullet points.



🍏 Draw a circuit diagram which includes: one battery, one voltmeter, one ammeter and two bulbs in series.

🍏 Draw a circuit diagram which includes: one battery, one voltmeter, one ammeter and two bulbs in parallel.

🍏 Recall the two factors which affect the resistance of an electrical circuit. For each one, outline *how* it affects the resistance.

1.
.....

2.
.....

🍏 What does an ammeter measure, and what are the units? (there are two words that can be used interchangeably here, give them both)

.....

🍏 What does a voltmeter measure, and what are the units?

.....

🍏 What does a resistor measure, and what are the units?

.....

🍏 What piece of equipment is used to measure length?

.....

- 🍏 Recall the equation that links the size of the electric current and the flow of electrical charge below.
Give the units for each part of the equation.

- 🍏 Recall the equation that links potential difference, current and resistance below.
Give the units for each part of the equation.

- 🍏 Which equation is used to represent a linear relationship?

.....